

# Computer Architecture

## Mid Term Exam

Name: \_\_\_\_\_

Instructions:

1. You can consult your notes but cannot ask for help to other students.
  2. Calculators are allowed.
  3. Time allowed is 1 hour 30 minutes. Marks will be deducted for late submission.
  4. Total weightage of this exam is 30 marks.
- 

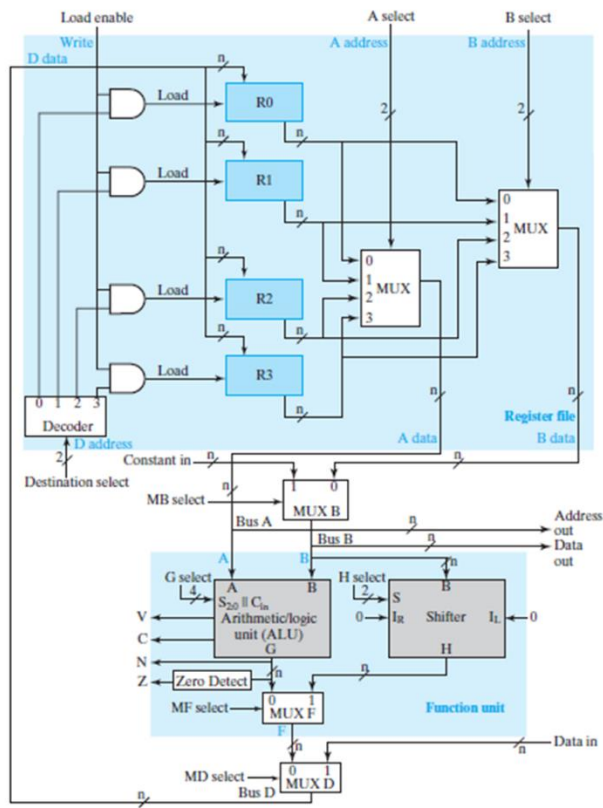


Figure 1

Q. 1 Refer to figure 1 and describe how this CPU will do memory operation (reading from memory and writing to memory)? (2 marks)

Q. 2 Refer to figure 1 and describe the function of control signals Load Enable and Destination Select? (2 marks)

Q. 3 Refer to figure 1 and mention the changes in terms of control signals that need to make to have 8 registers? (3 mark)

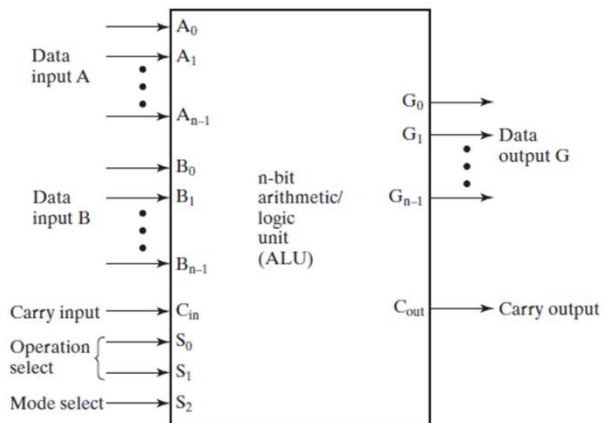


Figure 2

Q.4 Refer to figure 2 and relate the signals in figure 2 with signals in figure 1. Example is given below (4 marks)

Figure 2 Signals	Figure 1 Signals
Data input A	Bus A or A
Data input B	
Carry input	
Operation select S0	
Operation select S1	
Mode select	
Data output G	
Carry output	

Q.5 What binary values are required on inputs Cin, S1 and S2 to subtract number “B” from number “A” in figure 3? (2 mark)

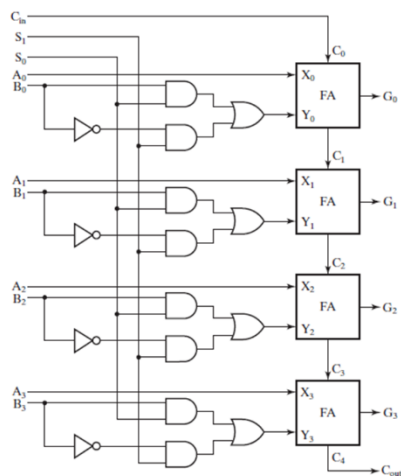


Figure 3

Signal	Value
Cin	
S1	
S2	

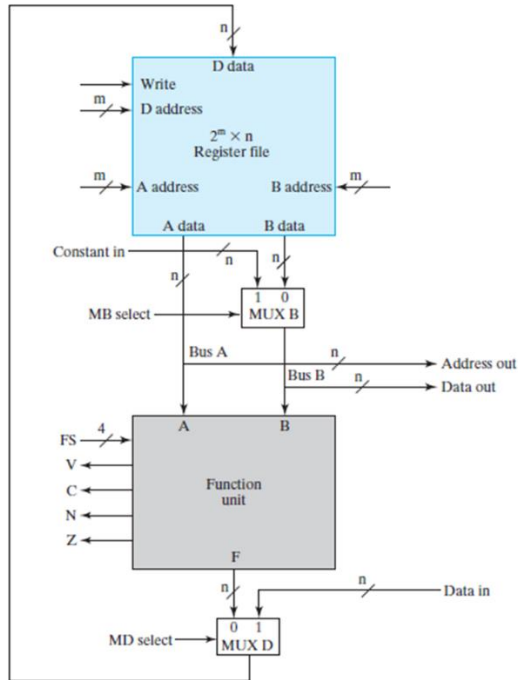


Figure 4

Q.6 Refer to figure 4 and answer below (4marks):

A. For having a 16 registers with each register of 16 bits, how many flipflops would be required?

\_\_\_\_\_

B. For having a 16 registers with each register of 16 bits, how many bits would be required in B Address? \_\_\_\_\_

C. How many different functions can be done by the Function Unit? \_\_\_\_\_

D. The purpose of Mux D is \_\_\_\_\_.

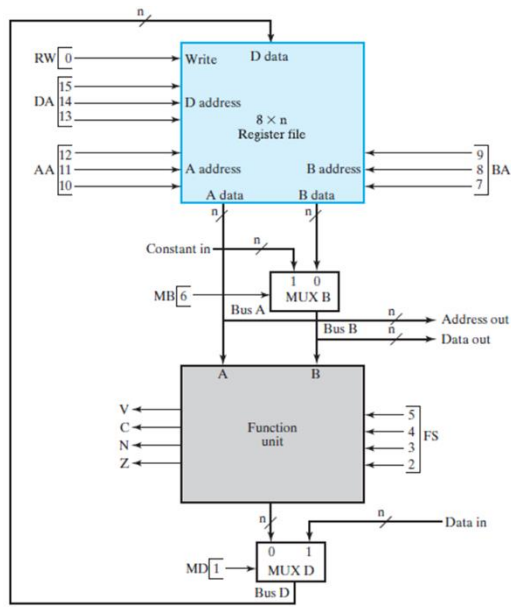


Figure 5

Q.7 Refer to figure 5, write the control word for the following instructions (6 marks)

$R3 = R2 + R1$

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

$R4 = R6 - R5$

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Q.8 What is the purpose of register "PC" and how it works (3 marks)?

Q.9 Explain the purpose of following instruction format and how it works?

15	9	8	6	5	3	2	0
Opcode		Address (AD) (Left)		Source reg- ister A (SA)		Address (AD) (Right)	