

# Computer Architecture

## A Generic CPU-2 Control Unit and ALU

Dr. Masood Mir

Week 4

# Control Unit

- The control unit for the datapath directs the information flow through the buses, the ALU, the shifter, and the registers by applying signals to the select inputs.

- For example, to perform the microoperation

$R1 \leftarrow R2 + R3$

- the control unit must provide binary selection values to the following sets of control inputs:
  1. A select, to place the contents of R2 onto A data and, hence, Bus A.
  2. B select, to place the contents of R3 onto the 0 input of MUX B; and MB select, to put the 0 input of MUX B onto Bus B.
  3. G select, to provide the arithmetic operation  $A + B$ .
  4. MF select, to place the ALU output on the MUX F output.
  5. MD select, to place the MUX F output onto Bus D.
  6. Destination select, to select R1 as the destination of the data on Bus D.
  7. Load enable, to enable a register—in this case, R1—to be loaded.


# Time Delay

- The sets of input values must be generated and must become available on the corresponding control lines early in the clock cycle.
- The binary data from the two source registers must propagate through the multiplexers and the ALU and on into the inputs of the destination register, all during the remainder of the same clock cycle.
- Then, when the next positive clock edge arrives, the binary data on Bus D is loaded into the destination register.
- To achieve fast operation, the ALU and shifter are constructed with combinational logic having a limited number of levels.

# Arithmetic Logic Unit

- The ALU is a combinational circuit that performs a set of basic arithmetic and logic microoperations.
- It has a number of selection lines used to determine the operation to be performed.
- The selection lines are decoded within the ALU, so that  $k$  selection lines can specify up to  $2^k$  distinct operations.
- Figure shows the external connections for a typical  $n$ -bit ALU.
- The  $n$  data inputs from A and the  $n$  data inputs from B provide the two operands to generate the result of an operation at the  $G$  outputs.
- The mode-select input  $S_2$  distinguishes between arithmetic and logic operations.
- The two Operation select inputs  $S_1$  and  $S_0$  and the Carry input  $C_{in}$  specify the 8 (eight) arithmetic operations with  $S_2$  at 0.
- Operand select input  $S_0$  and  $C_{in}$  specify the four logic operations with  $S_2$  at 1.
- We will discuss the design of this ALU in three stages. First, we design the arithmetic section. Then we design the logic section, and finally, we combine the two sections to form the ALU.



# Arithmetic Logic Unit

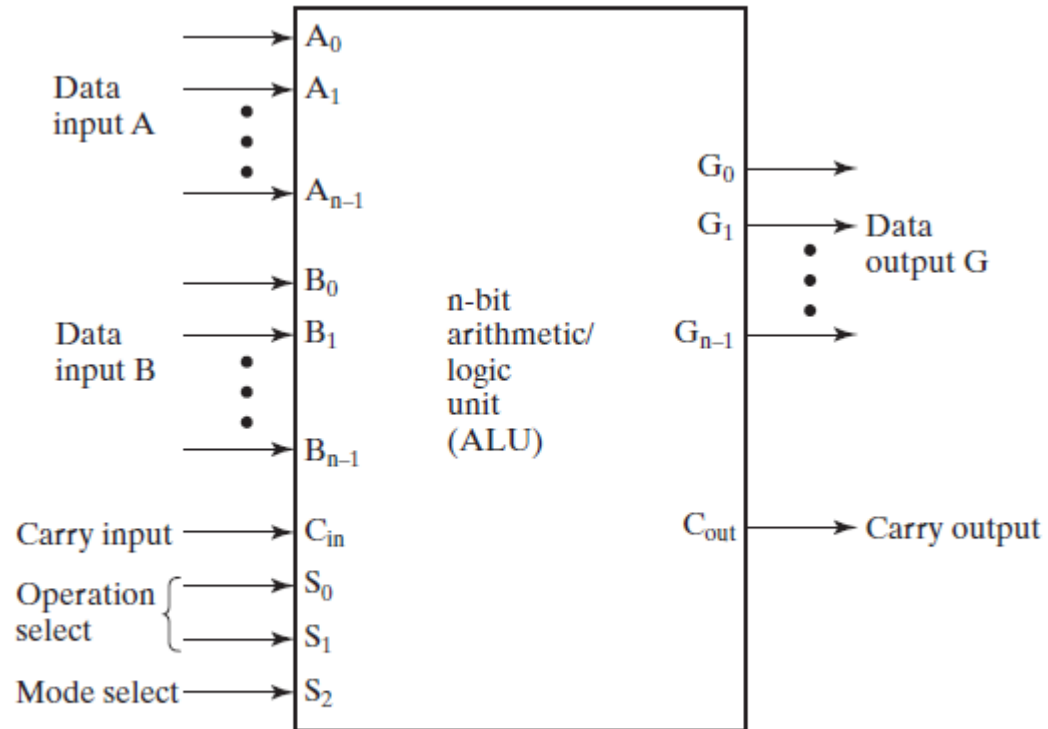

□ **FIGURE 8-2**  
Symbol for an  $n$ -Bit ALU

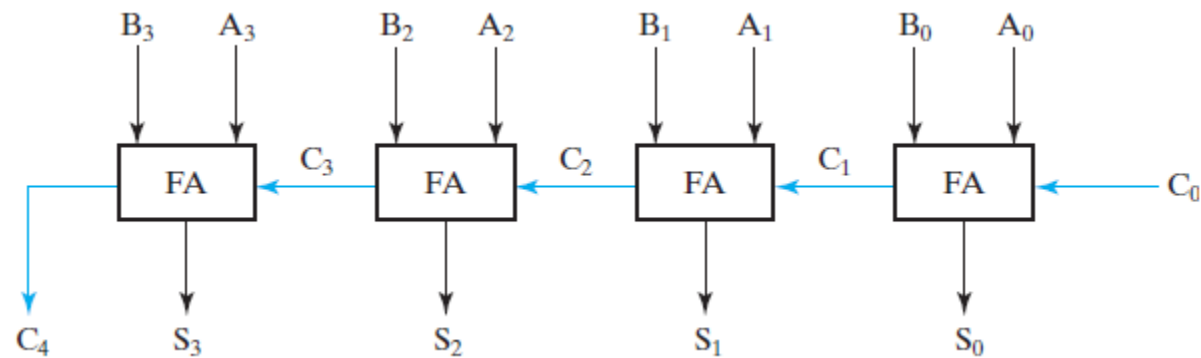 
# Arithmetic Circuit

- The basic component of an arithmetic circuit is a parallel adder, which is constructed with a number of full-adder circuits connected in cascade, as discussed in DLD.



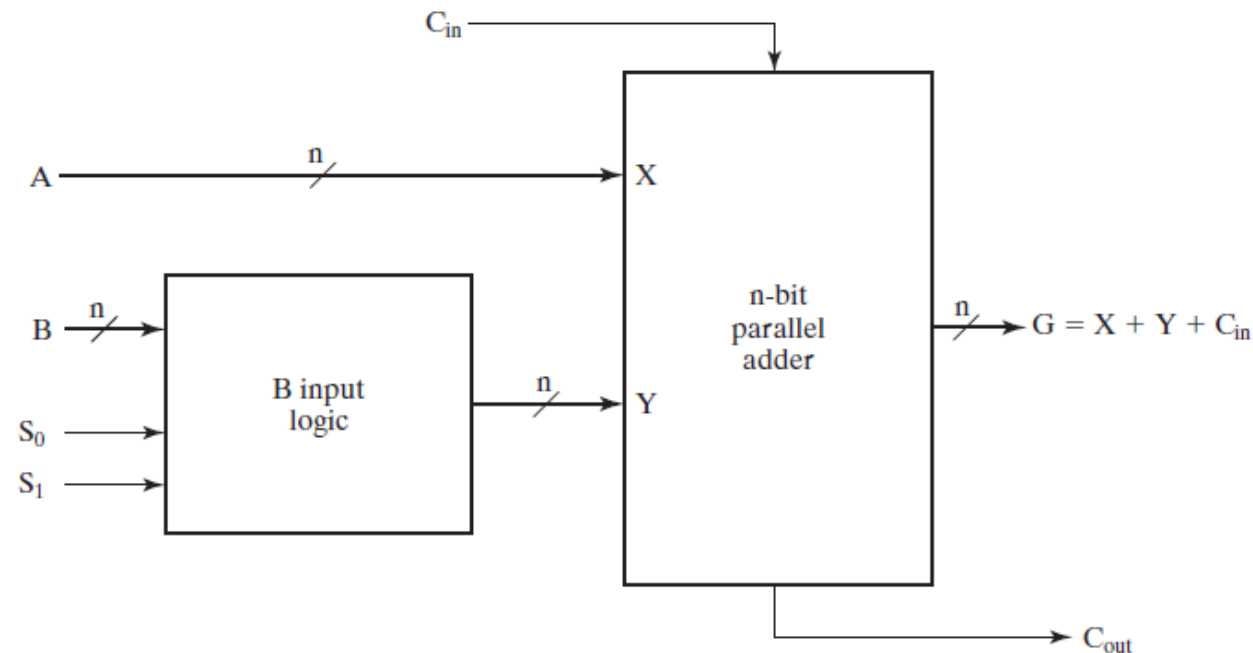
# Arithmetic Circuit

- By controlling the data inputs to the parallel adder, it is possible to obtain different types of arithmetic operations.
- The block diagram in Figure demonstrates a configuration in which one set of inputs to the parallel adder is controlled by the select lines  $S_1$  and  $S_0$ .
- There are  $n$  bits in the arithmetic circuit, with two inputs  $A$  and  $B$  and output  $G$ . The  $n$  inputs from  $B$  go through the  $B$  input logic to the  $Y$  inputs of the parallel adder.
- The output of the parallel adder is calculated from the arithmetic sum as  $G = X + Y + C_{in}$


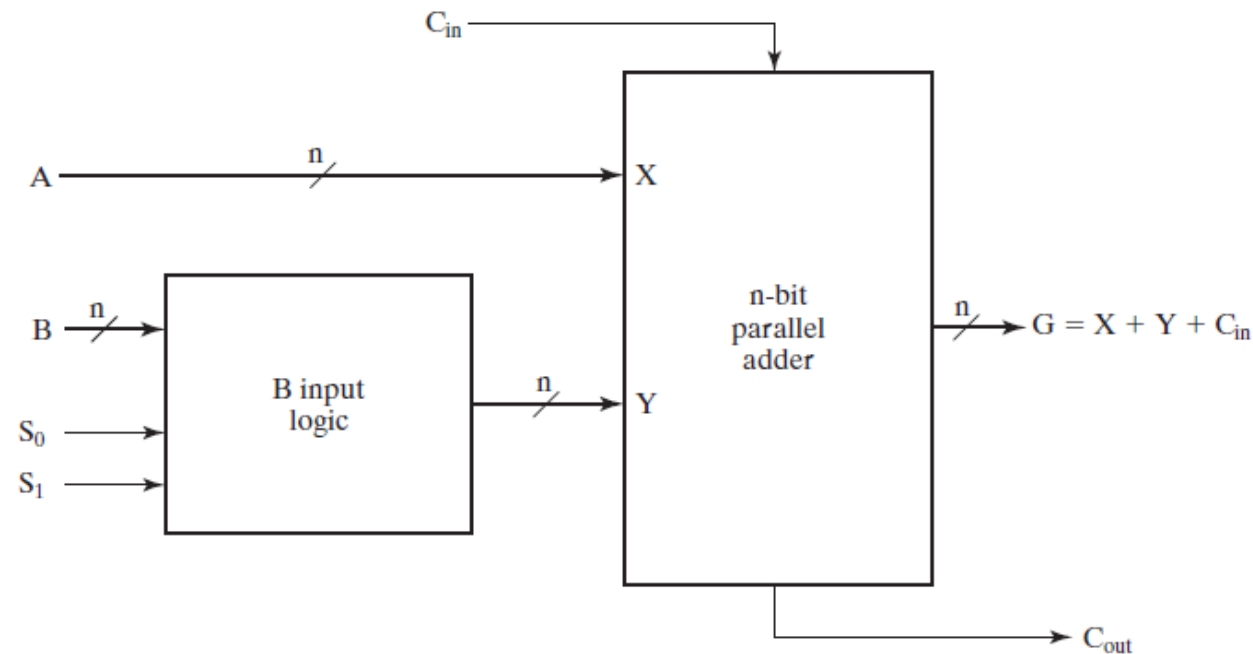
# Arithmetic Circuit


- By controlling the data inputs to the parallel adder, it is possible to obtain different types of arithmetic operations.
- The block diagram in Figure demonstrates a configuration in which one set of inputs to the parallel adder is controlled by the select lines  $S_1$  and  $S_0$ .
- There are  $n$  bits in the arithmetic circuit, with two inputs  $A$  and  $B$  and output  $G$ . The  $n$  inputs from  $B$  go through the  $B$  input logic to the  $Y$  inputs of the parallel adder.




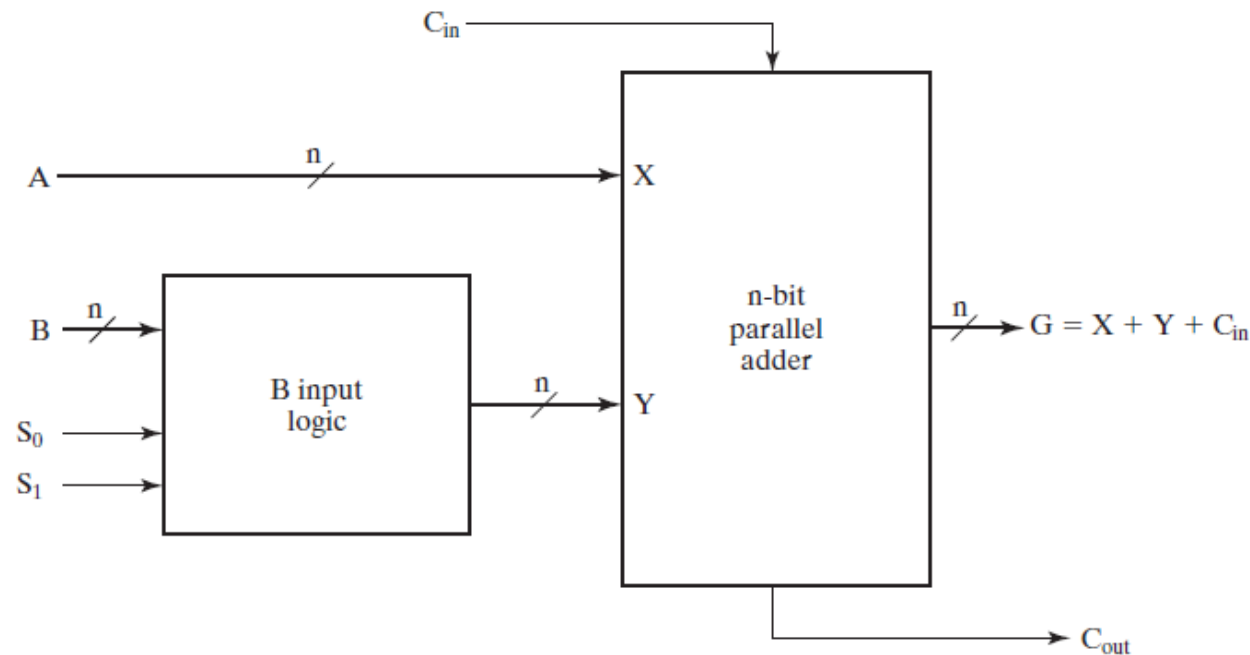
# Arithmetic Circuit

- The output of the parallel adder is calculated from the arithmetic sum as  $G = X + Y + C_{in}$
- where  $X$  is the  $n$ -bit binary number from the inputs and  $Y$  is the  $n$ -bit binary number from the  $B$  input logic.  $C_{in}$  is the input carry, which equals 0 or 1.
- Note that the symbol  $+$  in the equation denotes arithmetic addition and not OR logic.



# Arithmetic Circuit

- Table shows the arithmetic operations that are obtainable by controlling the value of Y with the two selection inputs S1 and S0.
- If the inputs from B are ignored and we insert all 0s at the Y inputs, the output sum becomes  $G = A + 0 + C_{in}$ . This gives  $G = A$  when  $C_{in} = 0$  and  $G = A + 1$  when  $C_{in} = 1$ . In the first case, we have
- a direct transfer from input A to output G. In the second case, the value of A is incremented
- by 1.
- For a straight arithmetic addition, it is necessary to apply the B inputs to the Y inputs of the parallel adder. This gives  $G = A + B$  when  $C_{in} = 0$ .

□ **TABLE 8-1**  
**Function Table for Arithmetic Circuit**

Select		Input	$G = (A + Y + C_{in})$	
$S_1$	$S_0$	Y	$C_{in} = 0$	$C_{in} = 1$
0	0	all 0s	$G = A$ (transfer)	$G = A + 1$ (increment)
0	1	B	$G = A + B$ (add)	$G = A + B + 1$
1	0	$\overline{B}$	$G = A + \overline{B}$	$G = A + \overline{B} + 1$ (subtract)
1	1	all 1s	$G = A - 1$ (decrement)	$G = A$ (transfer)

# Arithmetic Circuit

- Arithmetic subtraction is achieved by applying the complement of inputs B to the Y inputs of the parallel adder, to obtain  $G = A + B + 1$  when  $C_{in} = 1$ . This gives A plus the 2s complement of B, which is equivalent to 2s complement subtraction.
- All 1s is the 2s complement representation for -1. Thus, applying all 1s to the Y inputs with  $C_{in} = 0$  produces the decrement operation  $G = A - 1$ .

□ **TABLE 8-1**  
**Function Table for Arithmetic Circuit**

Select		Input	$G = (A + Y + C_{in})$	
$S_1$	$S_0$	Y	$C_{in} = 0$	$C_{in} = 1$
0	0	all 0s	$G = A$ (transfer)	$G = A + 1$ (increment)
0	1	B	$G = A + B$ (add)	$G = A + B + 1$
1	0	$\overline{B}$	$G = A + \overline{B}$	$G = A + \overline{B} + 1$ (subtract)
1	1	all 1s	$G = A - 1$ (decrement)	$G = A$ (transfer)

# Arithmetic Circuit

- The B input logic in Figure can be implemented with n multiplexers. The data inputs to each multiplexer in stage i for  $i = 0, 1, \dots, n - 1$  are 0,  $B_i$ ,  $B_i$ , and 1, corresponding to selection values  $S_1S_0$ : 00, 01, 10, and 11, respectively.
- Thus, the arithmetic circuit can be constructed with n full adders and n 4-to-1 multiplexers.
- The number of gates in the B input logic can be reduced if, instead of using 4-to-1 multiplexers, we go through the logic design of one stage (one bit) of the B input logic.
- This can be done by K-map as shown in Figure

Inputs			Output
$S_1$	$S_0$	$B_i$	$Y_i$
0	0	0	0 $Y_i = 0$
0	0	1	0
0	1	0	0 $Y_i = B_i$
0	1	1	1
1	0	0	1 $Y_i = \overline{B_i}$
1	0	1	0
1	1	0	1 $Y_i = 1$
1	1	1	1

(a) Truth table

	$S_0$			
	00	01	11	10
$S_1$ 0			1	
1	1		1	1
	$B_i$			

(b) Map simplification:  
 $Y_i = B_i S_0 + \overline{B_i} S_1$

# Arithmetic Circuit

- The truth table for one typical stage  $i$  of the logic is given in Figure (a).
- The inputs are  $S_1$ ,  $S_0$ , and  $B_i$ , and the output is  $Y_i$ .
- Following the requirements specified in Table 8-1, we let  $Y_i = 0$  when  $S_1S_0 = 00$ , and similarly assign the other three values of  $Y_i$  for each of the combinations of the selection variables.
- Output  $Y_i$  is simplified in the map in Figure 8-4(b) to give  $Y_i = B_iS_0 + \overline{B_i}S_1$ .
- where  $S_1$  and  $S_0$  are common to all  $n$  stages. Each stage  $i$  is associated with input  $B_i$  and output  $Y_i$  for  $i = 0, 1, 2, \dots, n-1$ .

Inputs			Output
$S_1$	$S_0$	$B_i$	$Y_i$
0	0	0	0 $Y_i = 0$
0	0	1	0
0	1	0	0 $Y_i = B_i$
0	1	1	1
1	0	0	1 $Y_i = \overline{B_i}$
1	0	1	0
1	1	0	1 $Y_i = 1$
1	1	1	1


(a) Truth table

		$S_0$			
		00	01	11	10
$S_1$	0			1	
	1	1		1	1
		$B_i$			

(b) Map simplification:  
 $Y_i = B_iS_0 + \overline{B_i}S_1$
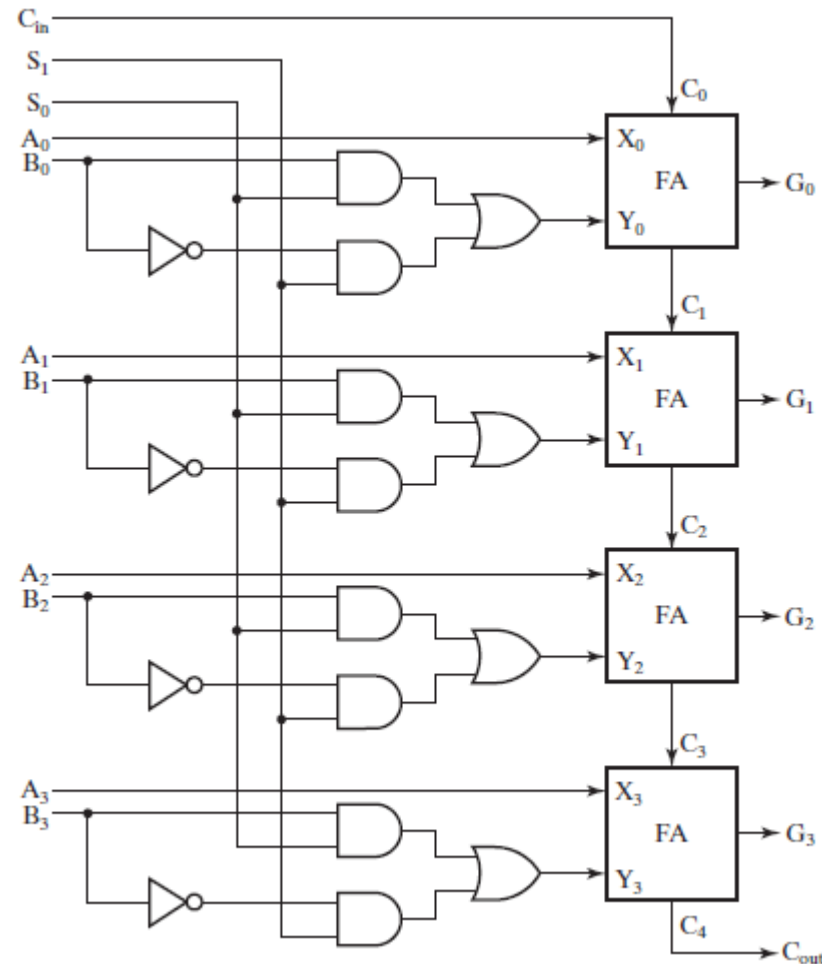
# Arithmetic Circuit

- Next Figure shows the logic diagram of an arithmetic circuit for  $n = 4$ . The four full-adder (FA) circuits constitute the parallel adder. The carry into the first stage is the input carry  $C_{in}$ . All other carries are connected internally from one stage to the next.



# Arithmetic Circuit

- Next Figure shows the logic diagram of an arithmetic circuit for  $n = 4$ . The four full-adder (FA) circuits constitute the parallel adder. The carry into the first stage is the input carry  $C_{in}$ . All other carries are connected internally from one stage to the next.

